
Assignment -1 Smart Home

Date	29 September 2022
Student Name	Manoj Kumar S
Student Roll No	911719104031
Maximum Marks	2 Marks

Question-1:

Build a smart home in Thinkercad with 2 sensors, an Led, buzzer and submit it

Output:

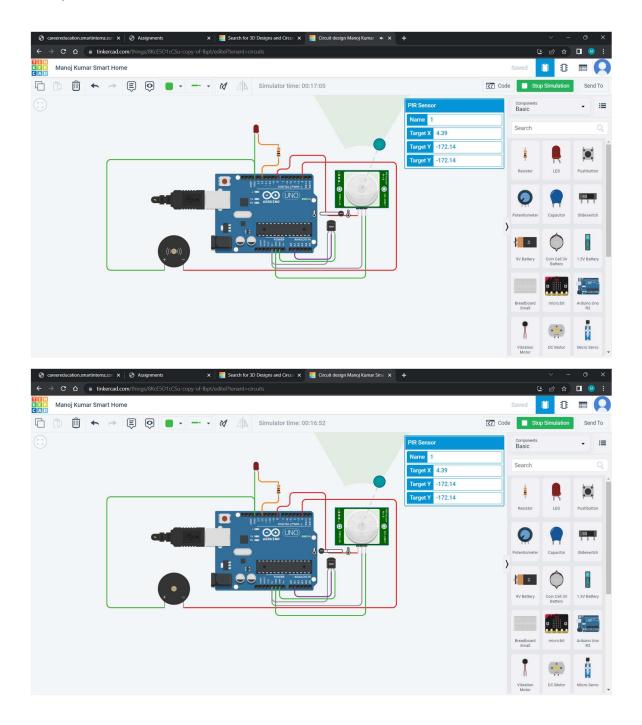

Screenshot:

